



CURRENT TO VOLTAGE CONVERTER AND VOLTAGE TO CURRENT CONVERTER

PRESENTED BY TEAM 6

RAHUL SAJNANI – 20171056

ANOUSHKA VYAS – 20171057

AJAY SHRIHARI - 20171097

SAUMYA SHAH – 20171193

DESIGN AND WORKING


To make a voltage to current converter or vice versa we use an operational amplifier.

One may ask why do we need an operational amplifier instead of just connecting a voltage source and resistor in series.


In this case the current across the load will depend on its overall impedance.

Now we will show you how we can use the op amp in this case.

Voltage to current converter

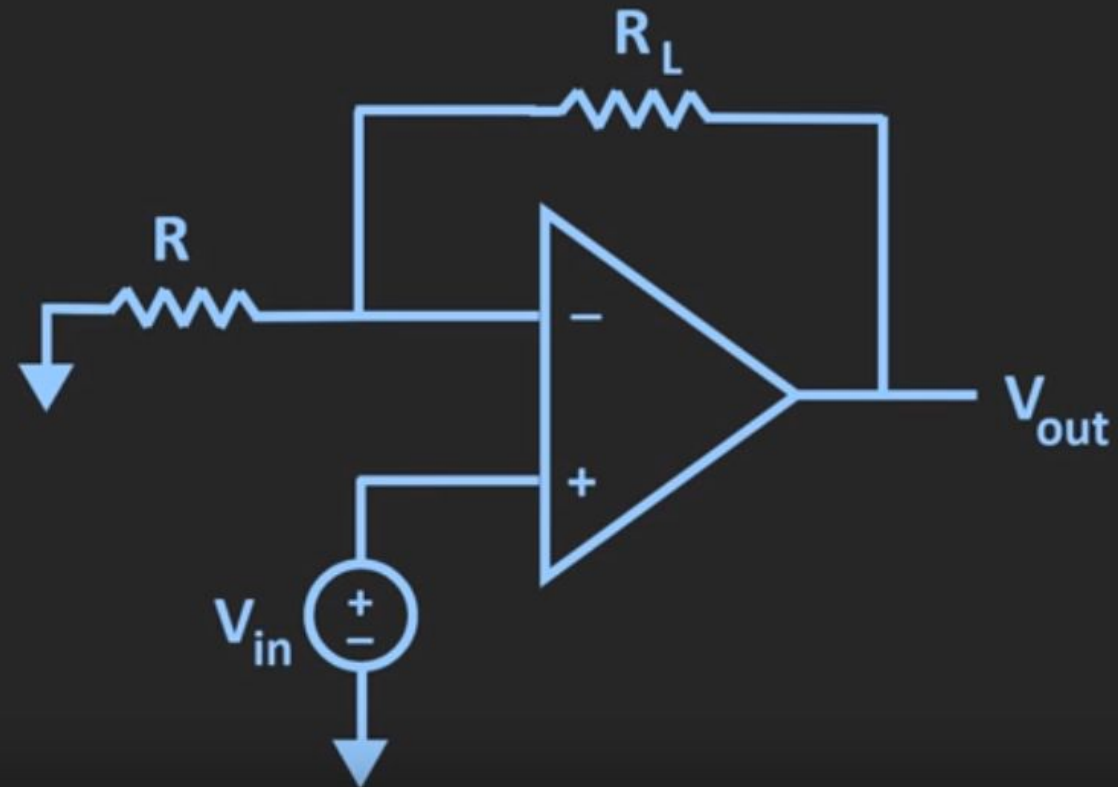

CURRENT TO VOLTAGE CONVERTER

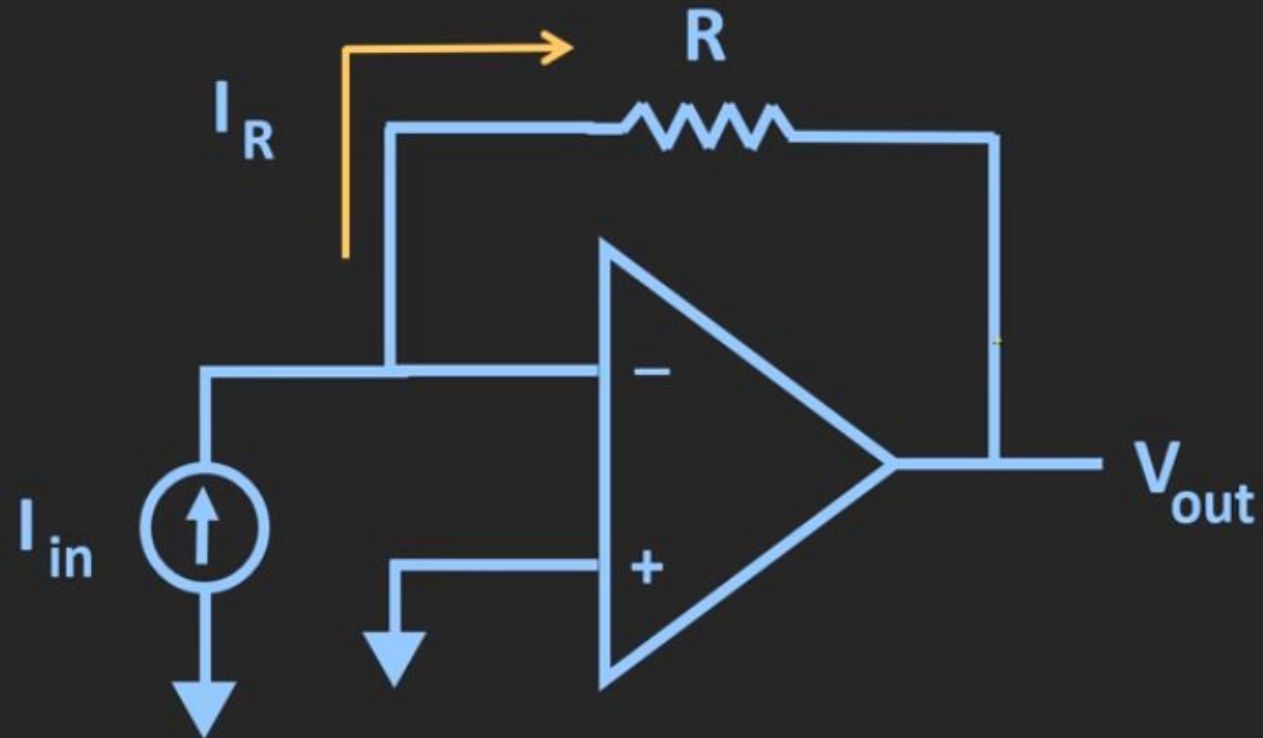

DESIGNING AN OPERATIONAL AMPLIFIER


We have many stages in an operational amplifier.

The main aim of an amplifier is to have :



- ▶ High input impedance
- ▶ High gain
- ▶ Low output impedance

In the coming slides we will explain how we deal with each stage.


The Design

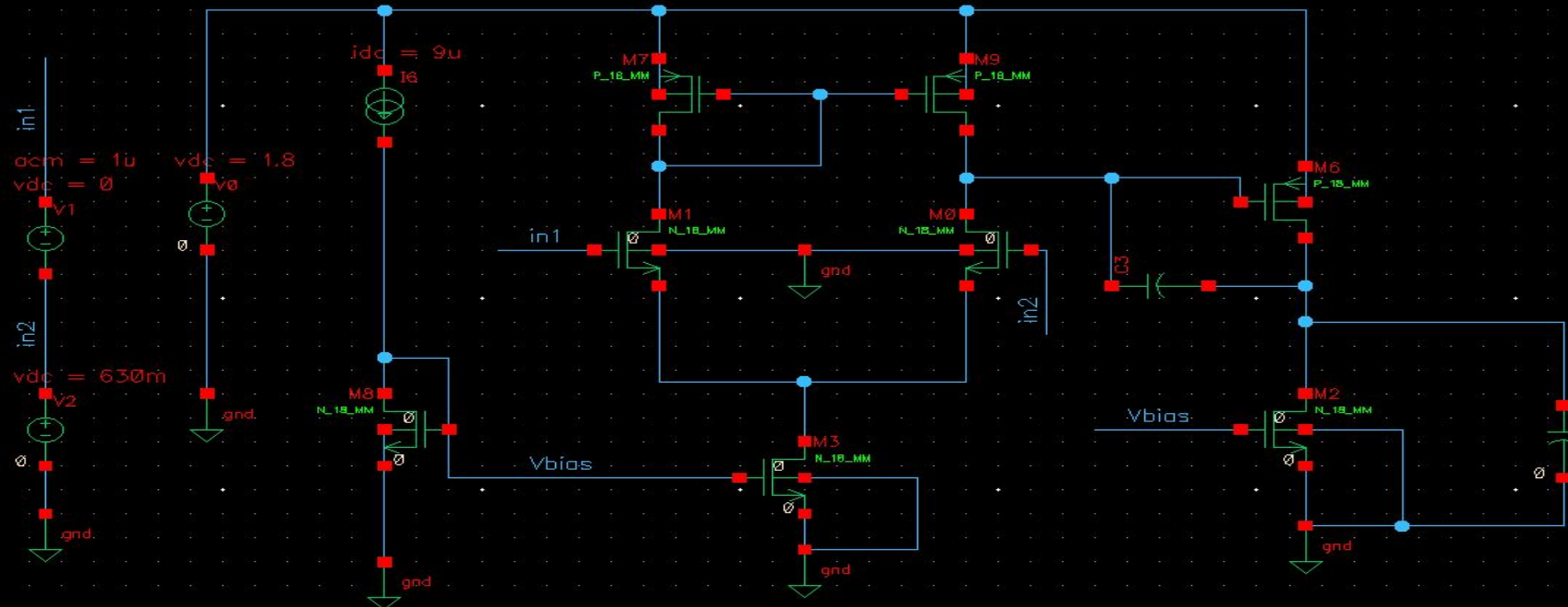

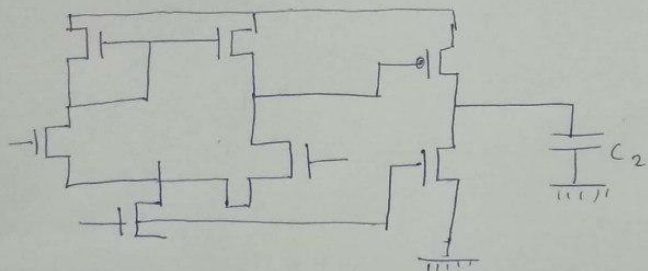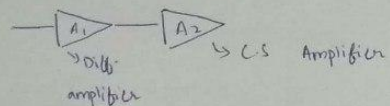Differential Amplifier cannot provide enough gain.




Small signal model

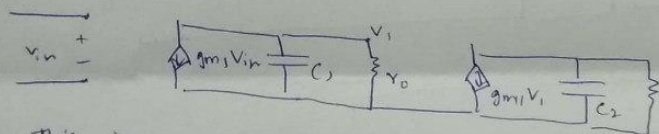

This is a 2 port system.



$$P_1 = \frac{1}{r_{O1} C_1} ; P_2 = \frac{1}{r_{O2} C_2}$$

Now, we draw the Bode plot.

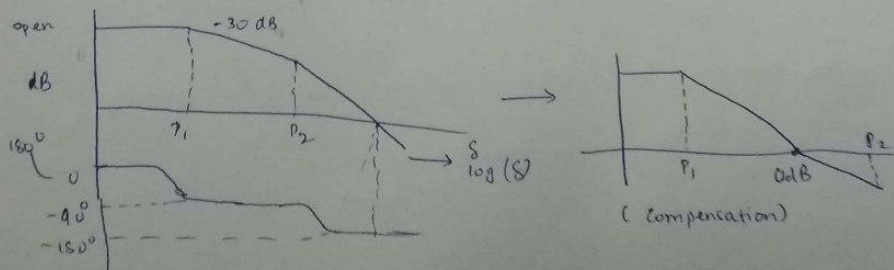



There is a problem with the phase margin (must be $\geq 45^\circ$)
For this, we do compensation and move the domain pole.

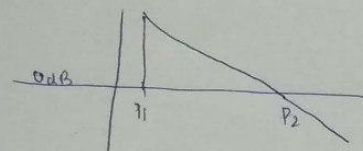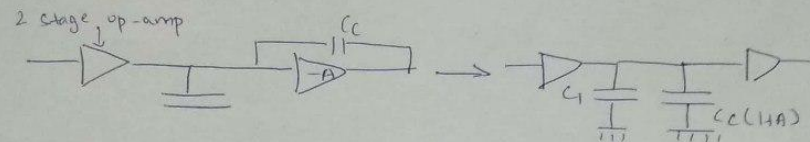To move P_1 , increase C_1 , and to avoid a large capacitor, we use the Miller Effect.



$$P_1 = \frac{1}{r_{O1} [C_1 + C_c (1+A)]}$$

New Circuit Diagram

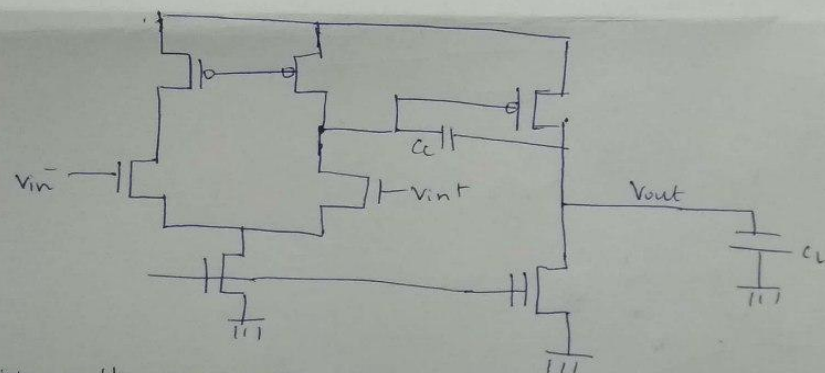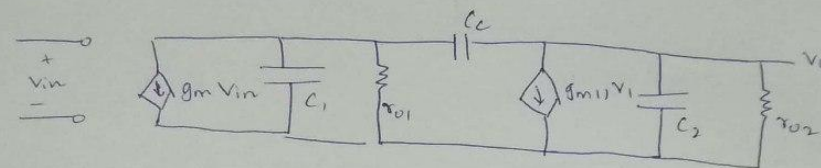

We can't use miller theorem because of pole splitting

$$\text{Method to find } \frac{V_O}{V_{in}} \Rightarrow \frac{V_1 \times V_O}{V_{in} V_1}$$

$$\frac{V_1}{V_{sc1}} + \frac{V_1}{R_1} + g_{m1} V_{in} + \frac{V_1 - V_O}{V_{sc2}} = 0$$

$$V_1 (sC_1 + \frac{1}{R_1} + sC_c) + g_{m1} V_{in} - V_O sC_c = 0$$

$$V_1 = \frac{V_0 \cdot sC_c R_1 - g_{m1} R_1 V_{in}}{1 + sR_1(C_1 + C_c)} \dots (1)$$

Node analysis @ V_0

$$\frac{V_0}{sC_c} + \frac{V_0}{R_2} + g_{m2} V_1 + \frac{V_0 - V_1}{sC_c} = 0$$

$$V_0 [s(C_c + C_2) + 1/R_2] = V_1 [sC_c - g_{m2}]$$

substitute (1) (V_1 value)

$$V_0 [s(C_c + C_2) + 1/R_2] = \frac{(V_0 sC_c R_1 - g_{m1} R_1 V_{in})(sC_c - g_{m2})}{1 + s(C_1 + C_c)R_1}$$

$$V_0 [s(C_c + C_2)R_2 + 1] [1 + s(C_1 + C_c)R_1] = (V_0 sC_c R_1 - g_{m1} R_1 V_{in})(sC_c - g_{m2})$$

$$\frac{V_0}{V_{in}} = \frac{g_{m1} R_1 \cdot g_{m2} R_2 \left(1 - \frac{sC_c}{g_{m2}}\right)}{s^2 [R_1 R_2 (C_1 C_2 + C_1 C_c + C_2 C_c)] + s [R_2 (C_c + C_2) + R_1 (C_c + C_1) + C_c g_{m2} R_2] + 1}$$

Assume

$$\frac{V_0}{V_{in}} = \frac{A_{DC} \left(1 - \frac{s}{\omega_z}\right)}{(1 + s/p_1)(1 + s/p_2)} = \frac{A_{DC} \left(1 - \frac{s}{\omega_z}\right)}{1 + s \left(\frac{1}{p_1} + \frac{1}{p_2}\right) + s^2 \left(\frac{1}{p_1 p_2}\right)}$$

$$s \left(\frac{1}{p_1} + \frac{1}{p_2}\right) \approx s \cdot \frac{1}{p_1}$$

$$p_1 \approx \frac{1}{R_2(C_c + C_2) + R_1(C_c + C_1) + g_{m2} R_2 R_1 C_c}$$

$$p_1 \approx \frac{1}{g_{m2} R_2 R_1 C_c} ; \text{ (1st pole)}$$

$$p_1 p_2 = \frac{1}{R_1 R_2 (C_1 C_2 + C_1 C_c + C_2 C_c)} ;$$

$$p_2 = \frac{p_1 p_c}{p_1} = \frac{1}{\cancel{R_1 R_2} [C_1 C_2 + C_1 C_c + C_2 C_c]} \times g_{m2} \cancel{R_2} R_1 C_c$$

$$p_2 = \frac{g_{m2} C_c}{\underbrace{C_1 C_2 + C_1 C_c}_{\text{small - neglect}} + \underbrace{C_2 C_c}_{\text{big}}} \approx \frac{g_{m2} C_c}{C_2 \cdot C_c}$$

$$p_2 = \frac{g_{m2}}{C_2} ; \text{ (2nd pole)}$$

Using equations,

$$z = \frac{g_{m2}}{C_c} ; \quad p_1 = \frac{1}{g_{m2} R_1 R_2 C_c} ; \quad p_2 = \frac{g_{m2}}{C_2}$$

$$A_{DC} = g_{m1} R_1 \cdot g_{m2} R_2$$

$$GBW = DC \text{ gain} \times p_1$$

$$= \frac{g_{m1} R_1 \cdot g_{m2} R_2 \times 1}{g_{m2} R_1 R_2 C_c}$$

$$GBW = \frac{g_{m1}}{C_c} ;$$


Slew rate

(on next page)

For slew rate, M_1 is ON and M_2 is OFF

Slew rate

$$= \frac{I_0}{C_c}$$

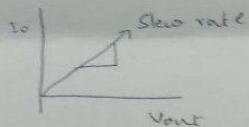


Second case

M_2 is ON, M_1 is OFF

I_0 flows through M_u because of current mirror

To flows through Ce

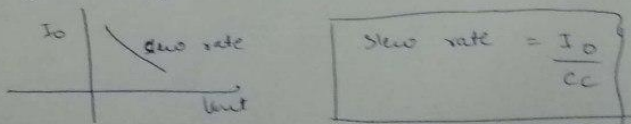

⑤

slow rate GBW $\frac{g_m}{C_c}$

$$Z = \frac{q_m v}{C_c}$$

P_C gain $\times P_1$

$$g_{m1} g_{m2} \cdot R_{o1} \cdot R_{o2}$$

Assumption

$$10 \text{ GBW} = z$$

$$\frac{A_{DL}(1-\frac{s}{z})}{(1+\frac{s}{p_1})(1+\frac{s}{p_2})}$$

carrier
bandwidth is freq

$$\frac{v_0}{v_{in}} = -\tan^{-1}\left(\frac{\omega}{2}\right) - \tan^{-1}\left(\frac{\omega}{p_1}\right) - \tan^{-1}\left(\frac{\omega}{p_2}\right)$$

$$z \approx 10 \text{ GHz}$$

$$= \tan^{-1}\left(\frac{C_1 B W}{Z}\right) = \tan^{-1}\left(\frac{C_1 B W}{P_1}\right) = \tan^{-1}\left(\frac{C_1 B W}{P_2}\right)$$

$$= \tan^{-1}\left(\frac{1}{10}\right) = \tan^{-1}\left(\frac{g m_1}{g_c} \frac{g m_2 R_1 R_2}{g_c g m_2}\right) = \tan^{-1}\left(\frac{g m_1}{g_c} \frac{1}{g m_2}\right)$$

$$\angle \frac{v_o}{v_i} = -\tan^{-1}\left(\frac{1}{10}\right) - \tan^{-1}(A_{DC}) - \tan^{-1}\left(\frac{A_{BW}}{P_L}\right)$$

$$-5.710 \quad -89.98 \quad -1 \text{ cm}^{-1}$$

$$-120 = -5.71 - 89.98 - 120^{-1} \left(\frac{C_{1BW}}{P_2} \right)$$

$$\tan^{-1}\left(\frac{GBW}{P_i}\right) = 24.31$$


$$\frac{C_{10W}}{P_2} = \tan(24.37) = 0.4513$$

$$P_2 = \frac{G B W}{0.4513} = \cancel{2.116} \quad 2.27 \text{ G B W}$$

$$P_1 = \frac{1}{\gamma m_2 R_1 R_2 C_C}$$

$$P_2 = \frac{g r n_1}{c_2}$$

-20 dB/dec.

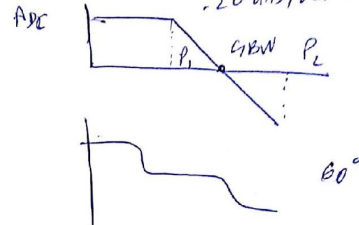

60°

$$\frac{g_{m1}}{C_L} \geq 7.2 \text{ GBW}$$

$$\frac{g_{m2}}{C_L} \geq 2.2 \frac{g_{m1}}{C_L}$$

C_L is cap in
second stage
 $= C_L$

$$A_3 \approx 10 \frac{g_{m1}}{C_L} \text{ GBW}$$

$$\frac{g_{m2}}{C_L} = \frac{10 g_{m1}}{C_L}$$

$$g_{m2} = 10 g_{m1}$$

$$\frac{10 g_{m1}}{C_L} \geq 2.2 \frac{g_{m1}}{C_L}$$

$$C_L \geq 0.22 C_L$$


$$\frac{10 C_L}{2.2} \geq C_L$$

$$\frac{q_p}{500 f}$$

$$\frac{q}{500} \times 10^6 \times 10^{13.9}$$

$$\frac{q}{500} \times 10^7$$

Design of 2-stage op amp

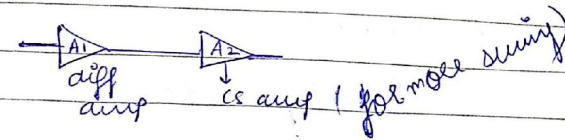

if we use pmos - more swing

$$\text{DC gain} - 3165 \approx 70 \text{ dB}$$

$$\text{GBW} = 30 \text{ MHz}$$

$$\text{PM} > 50^\circ$$

$$\text{Slew rate} = 20 \text{ V/}\mu\text{s}$$


$$I_{CMR(+)} = 1.6 \mu\text{A}$$

$$I_{CMR(-)} = 0.8 \mu\text{A}$$

$$C_L = 2 \text{ pF}$$

$$\text{Power} \leq 300 \mu\text{W}$$

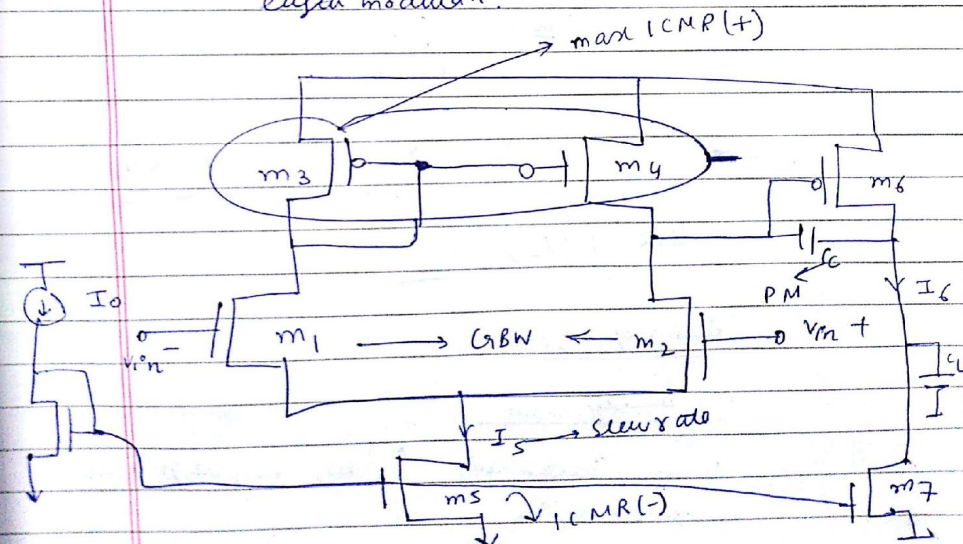use W/L in ratio to prevent channel length modulation.



classmate
Date
Page

$$C_c \gg 0.22 \text{ CL for PM } \approx 60$$

① $C_c \gg 420 \text{ fF}$
 \downarrow Taking 300 fF

② $3R = \frac{I_S}{C_c}$
 $I_S = 3R \cdot C_c = \frac{20 \text{ V}}{\mu\text{s}} \times 300 \text{ fF}$
 $= 10 \mu\text{A}$
 $I_S \approx 20 \mu\text{A}$

Taking $5 \mu\text{A}$

Design of M_1, M_2

$$g_{m1} = G_B \times C_c \times 2\pi$$

$$g_{m1} = 30 \mu\text{A/V} \times 300 \text{ fF} \times 2\pi$$

$$g_{m1} = 150.7 \mu\text{S}$$

$$g_{m1} = 150 \mu\text{S}$$

$$\left(\frac{W}{L}\right)_1 = \frac{g_{m1}^2}{\mu_{n\text{COX}} 2I_D}$$

$$= \frac{150^2}{300 \times 20} = 4.266$$

Use $(W/L)_{1,2} = 5$

Design of M_3 PM

M_3 always in sat

If we increase $V_{in} \uparrow$, M_1 might go into triode region

$$(V_D)_{M_1} > V_G - V_{t1}$$

$$V_G < (V_{D1})_{M_1} + V_{t1}$$

$$V_{Pn} < V_{D1} + V_{t1}$$

$$V_{Pn\text{max}} = V_{D1} + V_{t1}$$

$$V_{D1} = V_{DD} - (V_{SG})_{M_3}$$

$$I_3 = \frac{\mu_{p\text{COX}} (W/L)}{2} (V_{GS} - V_{t1})^2$$

$$V_{GS} = \sqrt{\frac{2I_3}{\beta_P}} + |V_{t3}|$$

$$V_{D1} = V_{DD} - \left[\sqrt{\frac{2I_3}{\beta_P}} + |V_{t3}| \right]$$

$$I_{CMR+} \leq V_{D1\text{min}} + V_{t1\text{min}}$$

$$V_{D1\text{min}} = V_{DD} - \left[\sqrt{\frac{2I_3}{\beta_P}} + |V_{t3}| \right]_{\text{min}}$$

$$\leq V_{DD} - \sqrt{\frac{2I_3}{\beta_P}} - |V_{t3}|_{\text{max}} + V_{t1\text{min}}$$

$$\mu_{p\text{COX}} = 60 \mu\text{S/V}$$

$$(W/L)_3 = \frac{2I_{D3}}{\mu_{p\text{COX}} [V_{DD} - I_{CMR+} - V_{t3\text{max}} + V_{t1\text{min}}]^2}$$

Using just diff amp
 with $(W/L)_3 = 20$, assuming

$$I_{D3} = 10 \mu$$

Putting

$$V_{t3max} = 0.51$$


$$V_{t1min} = 0.47$$

$$(W/L)_3 = \frac{2 \times 10 \mu}{60 \mu [1.8 - 1.6 - 0.51 + 0.47]^2}$$

$$= 13.02$$

using ≈ 14

design m5

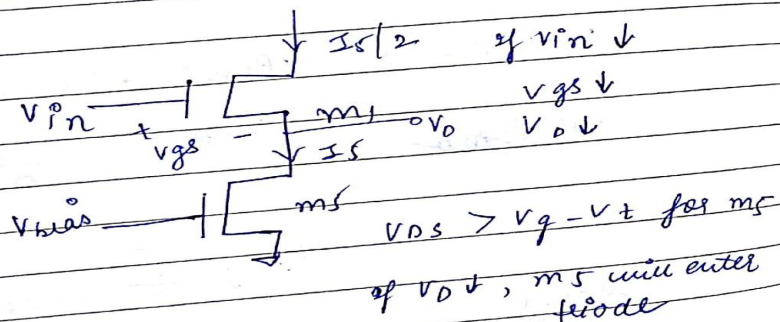

$$V_{in} > V_{gs1} + V_{Dsats}$$

$$I_{CMR} \approx \frac{V_{gs1} + V_{Dsats}}{\max}$$

$$ICMR = \frac{1}{\left[\sqrt{\frac{2I_{D1}}{\beta_1}} + V_{t1} \right] \max} + V_{Dsats}$$

$$V_{Dsats} \approx I_{CMR} - \sqrt{\frac{2I_{D1}}{\beta_1}} - V_{t1max}$$

$$V_{Dsats} \approx 0.8 - \sqrt{\frac{2 \times 10 \mu}{300 \mu \times 5}} - V_{t1max}$$

using per unit

$$V_{Dsats} = 0.8 - 0.1154 = 0.59$$

$$= 94.6 \text{ mV}$$

Should be 7, 100 mV

For saturation

But we can't increase $m5$

coz $m7$ will increase

So, we can't do that otherwise gain decrease.

So we have to decrease $(W/L)_4 \approx 6$

$$V_{Dsats} \approx 105 \text{ mV}$$

$$(W/L)_5 = \frac{2 \times 20 \mu}{300 \times (105 \text{ mV})^2}$$

$$= 12.09$$

$$(W/L)_5 \approx 12$$

design m6

$$g_{m6} \approx 10 \text{ gm}$$

$$g_{m6} \approx 10 \times 1600 = 1600 \mu$$

$$V_{Ds m3} = V_{Ds m4} = V_{Ds m6}$$

$$V_{Gs m3} = V_{Gs m4} = V_{Gs m6}$$

$$\frac{(W/L)_6}{(W/L)_4} = \frac{g_{m6}}{g_{m4}} \quad g_{m4} = \frac{60 \times 14 \times 2 \times 10}{1} = 169.61$$

$$(w/L)_6 = 172.82$$

$$\approx 173$$

m7

$$\frac{I_6}{I_4} = \frac{(w/L)_6}{(w/L)_4}$$

$$I_6 = 104.88$$

$$I_6 = 125 \mu A$$

$$\frac{I_7}{I_5} = \frac{(w/L)_7}{(w/L)_5} \quad \left\{ \begin{array}{l} m_5 - m_7 \text{ same} \\ \hline V_{GS} \end{array} \right.$$

$$(w/L)_7 = \underline{\underline{75}}$$